

Lab-5

(1) Implement BCD to seven-segment Decoder. (2) Implement 16x1 MUX using 2x1 Muxes only. (3) Implement 4x16 Decoder using 2x4 Decoders only.