

# Lab-8

- (a). Implement Ring and Jonson counters using D-FFs in VHDL.
- (b). Implement in VHDL the following:
  - (i) a parallel in and parallel out shift register,
  - (ii) a serial-in and serial out shift register.